



(a) Shift-register implementation

	C_4	C_3	C_2	C_1	C_0	$C_4 \approx C_3 \approx I$	$C_4 \approx C_1 \approx I$	$C_4 \approx I$	$I = \text{input}$	
Initial	0	0	0	0	0	1	1	1	1	} Message to be sent
Step 1	1	0	1	0	1	1	1	1	0	
Step 2	1	1	1	1	1	1	1	0	1	
Step 3	1	1	1	1	0	0	0	1	0	
Step 4	0	1	0	0	1	1	0	0	0	
Step 5	1	0	0	1	0	1	0	1	0	
Step 6	1	0	0	0	1	0	0	0	1	
Step 7	0	0	0	1	0	1	0	1	1	
Step 8	1	0	0	0	1	1	1	1	0	
Step 9	1	0	1	1	1	0	1	0	1	
Step 10	0	1	1	1	0					

(b) Example with input of 1010001101

Figure 6.6 Circuit with Shift Registers for Dividing by the Polynomial $X^5 + X^4 + X^2 + 1$